

1.4 THE CIRCUIT

Simply an electric circuit consists of three parts: (1) energy source, such as battery or generator, (2) the load or sink, such as lamp or motor, and (3) connecting wires as shown in Fig. 1.2. This arrangement represents a simple circuit. A battery is connected to a lamp with two wires. The purpose of the circuit is to transfer energy from source (battery) to the load (lamp). And this is accomplished by the passage of electrons through wires around the circuit.

The current flows through the filament of the lamp, causing it to emit visible light. The current flows through the battery by chemical action. A closed circuit is defined as a circuit in which the current has a complete path to flow. When the current path is broken so that current cannot flow, the circuit is called an open circuit.

More specifically, interconnection of two or more simple circuit elements (viz. voltage sources, resistors, inductors and capacitors) is called an electric network.

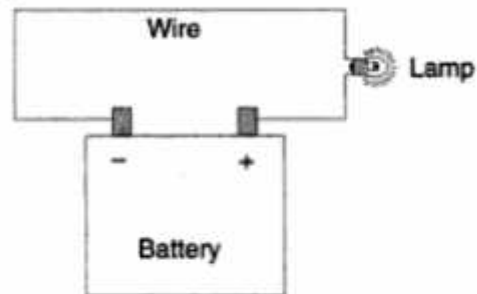


Fig. 1.2

If a network contains at least one closed path, it is called an electric circuit. By definition, a simple circuit element is the mathematical model of two terminal electrical devices, and it can be completely characterised by its voltage and current. Evidently then, a physical circuit must provide means for the transfer of energy.

Broadly, network elements may be classified into four groups, viz.

1. Active or passive
2. Unilateral or bilateral
3. Linear or nonlinear
4. Lumped or distributed

1.4.1 Active and Passive

Energy sources (voltage or current sources) are active elements, capable of delivering power to some external device. Passive elements are those which are capable only of receiving power. Some passive elements like inductors and capacitors are capable of storing a finite amount of energy, and return it later to an external element. More specifically, an active element is capable of delivering an average power greater than zero to some external device over an infinite time interval. For example, ideal sources are active elements. A passive element is defined as one that cannot supply average power that is greater than zero over an infinite time interval. Resistors, capacitors and inductors fall into this category.

1.4.2 Bilateral and Unilateral

In the bilateral element, the voltage-current relation is the same for current flowing in either direction. In contrast, a unilateral element has different relations between voltage and current for the two possible directions of current. Examples of bilateral elements are elements made of high conductivity materials in general. Vacuum diodes, silicon diodes, and metal rectifiers are examples of unilateral elements.

1.4.3 Linear and Nonlinear Elements

An element is said to be linear, if its voltage-current characteristic is at all times a straight line through the origin. For example, the current passing through a resistor is proportional to the voltage applied through it, and the relation is expressed as $V \propto I$ or $V = IR$. A linear element or network is one which satisfies the principle of superposition, i.e. the principle of homogeneity and additivity. An element which does not satisfy the above principle is called a nonlinear element.

1.4.4 Lumped and Distributed

Lumped elements are those elements which are very small in size and in which simultaneous actions takes place for any given cause at the same instant of time.

Typical lumped elements are capacitors, resistors, inductors and transformers. Generally the elements are considered as lumped when their size is very small compared to the wave length of the applied signal. Distributed elements, on the other hand, are those which are not electrically separable for analytical purposes. For example, a transmission line which has distributed resistance, inductance and capacitance along its length may extend for hundreds of miles.

1.5 RESISTANCE PARAMETER

When a current flows in a material, the free electrons move through the material and collide with other atoms. These collisions cause the electrons to lose some of their energy. This loss of energy per unit charge is the drop in potential across the material. The amount of energy lost by the electrons is related to the physical property of the material. These collisions restrict the movement of electrons. The property of a material to restrict the flow of electrons is called resistance, denoted by R . The symbol for the resistor is shown in Fig. 1.3.



Fig. 1.3

The unit of resistance is ohm (Ω). Ohm is defined as the resistance offered by the material when a current of one ampere flows between two terminals with one volt applied across it.

According to Ohm's law, the current is directly proportional to the voltage and inversely proportional to the total resistance of the circuit, i.e.

$$I = \frac{V}{R}$$

or
$$i = \frac{v}{R}$$

We can write the above equation in terms of charge as follows.

$$V = R \frac{dq}{dt}, \quad \text{or} \quad i = \frac{v}{R} = Gv$$

where G is the conductance of a conductor. The units of resistance and conductance are ohm (Ω) and mho (\mathcal{U}) respectively.

When current flows through any resistive material, heat is generated by the collision of electrons with other atomic particles. The power absorbed by the resistor is converted to heat. The power absorbed by the resistor is given by

$$P = vi = (iR)i = i^2 R$$

where i is the current in the resistor in amps, and v is the voltage across the resistor in volts. Energy lost in a resistance in time t is given by

$$W = \int_0^t p dt = pt = i^2 R t = \frac{v^2}{R} t$$

where v is the volts

R is in ohms

t is in seconds and

W is in joules

1.6 INDUCTANCE PARAMETER

A wire of certain length, when twisted into a coil becomes a basic inductor. If current is made to pass through an inductor, an electromagnetic field is formed. A change in the magnitude of the current changes the electromagnetic field. Increase in current expands the fields, and decrease in current reduces it. Therefore, a change in current produces change in the electromagnetic field, which induces a voltage across the coil according to Faraday's law of electromagnetic induction.

The unit of inductance is *henry*, denoted by *H*. By definition, the inductance is one henry when current through the coil, changing at the rate of one ampere per second, induces one volt across the coil. The symbol for inductance is shown in Fig. 1.4.

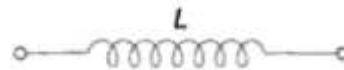


Fig. 1.4

The current-voltage relation is given by

$$v = L \frac{di}{dt}$$

where v is the voltage across inductor in volts, and i is the current through inductor in amps.

The power absorbed by inductor is

$$P = vi = Li \frac{di}{dt} \text{ watts}$$

The energy stored by the inductor is

$$\begin{aligned} W &= \int_0^t p dt \\ &= \int_0^t Li \frac{di}{dt} dt = \frac{Li^2}{2} \end{aligned}$$

From the above discussion, we can conclude the following.

1. The induced voltage across an inductor is zero if the current through it is constant. That means an inductor acts as short circuit to dc.
2. A small change in current within zero time through an inductor gives an infinite voltage across the inductor, which is physically impossible. In a fixed inductor the current cannot change abruptly.
3. The inductor can store finite amount of energy, even if the voltage across the inductor is zero, and
4. A pure inductor never dissipates energy, only stores it. That is why it is also called a non-dissipative passive element. However, physical inductors dissipate power due to internal resistance.

1.7 CAPACITANCE PARAMETER

Any two conducting surfaces separated by an insulating medium exhibit the property of a capacitor. The conducting surfaces are called *electrodes*, and the insulating medium is called *dielectric*. A capacitor stores energy in the form of an electric field that is established by the opposite charges on the two electrodes. The electric field is represented by lines of force between the positive and negative charges, and is concentrated within the dielectric. The amount of charge

per unit voltage that is capacitor can store is its capacitance, denoted by C . The unit of capacitance is *Farad* denoted by F . By definition, one Farad is the amount of capacitance when one coulomb of charge is stored with one volt across the plates. The symbol for capacitance is shown in Fig. 1.5.

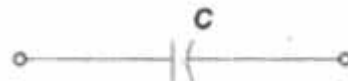


Fig. 1.5

A capacitor is said to have greater capacitance if it can store more charge per unit voltage and the capacitance is given by

$$C = \frac{Q}{V}, \quad \text{or} \quad C = \frac{q}{v}$$

(lower case letters stress instantaneous values)

We can write the above equation in terms of current as

$$i = C \frac{dv}{dt} \qquad \left(\because i = \frac{dq}{dt} \right)$$

where v is the voltage across capacitor, i is the current through it

The power absorbed by the capacitor is given by

$$p = vi = vC \frac{dv}{dt}$$

The energy stored by the capacitor is

$$W = \int_0^t p dt = \int_0^t vC \frac{dv}{dt} dt$$

$$W = \frac{1}{2} C v^2$$

1.13 Energy Sources

There are basically two types of energy sources ; voltage source and current source. These are classified as i) Ideal source and ii) Practical source.

Let us see the difference between ideal and practical sources.

1.13.1 Voltage Source

Ideal voltage source is defined as the energy source which gives constant voltage across its terminals irrespective of the current drawn through its terminals. The symbol for ideal voltage source is shown in the Fig. 1.14 (a). This is connected to the load as shown in Fig. 1.14 (b). At any time the value of voltage at load terminals remains same. This is indicated by V- I characteristics shown in the Fig. 1.14 (c).

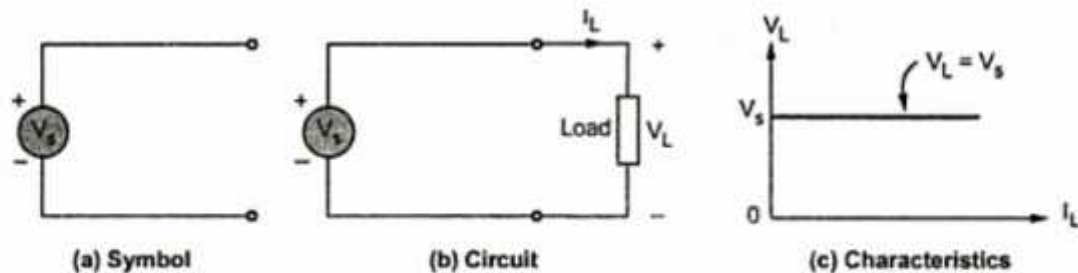


Fig. 1.14 Ideal voltage source

Practical voltage source :

But practically, every voltage source has small internal resistance shown in series with voltage source and is represented by R_{se} as shown in the Fig. 1.15.

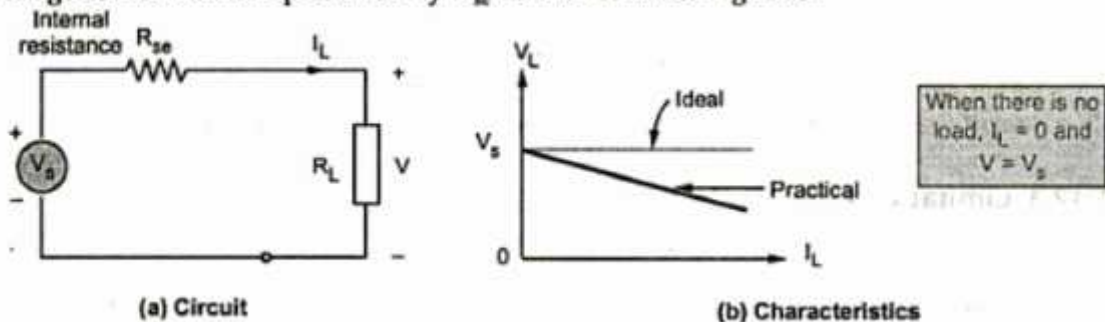


Fig. 1.15 Practical voltage source

Because of the R_{se} , voltage across terminals decreases slightly with increase in current and it is given by expression,

$$V_L = - (R_{se}) I_L + V_S = V_S - I_L R_{se}$$

Key Point: For ideal voltage source, $R_{se} = 0$

Voltage sources are further classified as follows,

i) **Time Invariant Sources :**


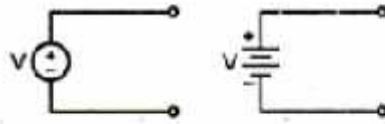


Fig. 1.16 (a) D. C. source

The sources in which voltage is not varying with time are known as **time invariant voltage sources** or **D.C. sources**. These are denoted by capital letters. Such a source is represented in the Fig. 1.16 (a).

ii) **Time Variant Sources :**

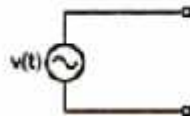

The sources in which voltage is varying with time are known as **time variant voltage sources** or **A.C. sources**.

1.13.2 Current Source

Ideal current source is the source which gives constant current at its terminals irrespective of the voltage appearing across its terminals. The symbol for ideal current source is shown in the Fig. 1.17 (a). This is connected to the load as shown in the Fig. 1.17 (b). At any time, the value of the current flowing through load I_L is same i.e. is irrespective of voltage appearing across its terminals. This is explained by V-I characteristics shown in the Fig. 1.17 (c).

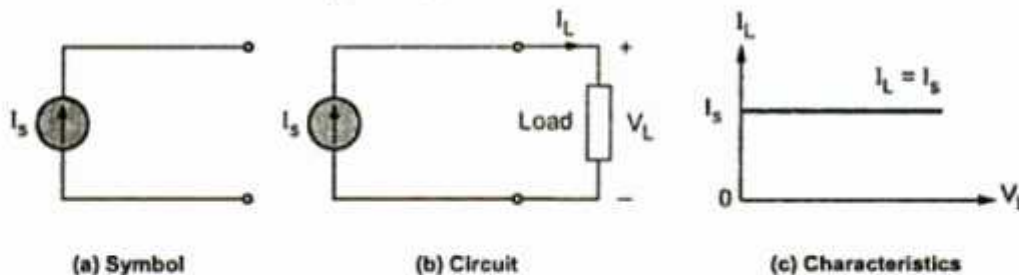


Fig. 1.17 Ideal current source

But practically, every current source has high internal resistance, shown in parallel with current source and it is represented by R_{sh} . This is shown in the Fig. 1.18.

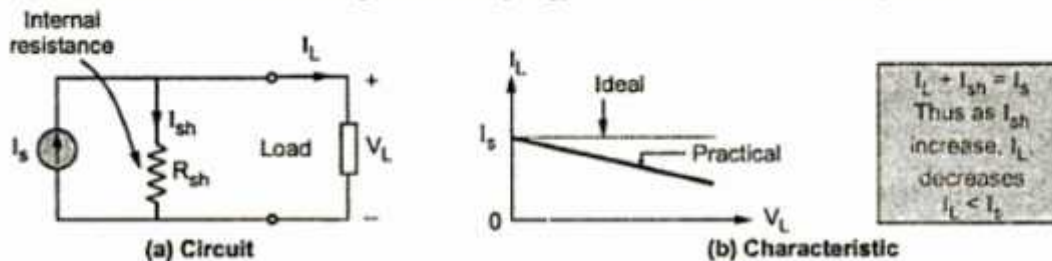


Fig. 1.18 Practical current source

Because of R_{sh} , current through its terminals decreases slightly with increase in voltage at its terminals.

Key Point: For ideal current source, $R_{sh} = \infty$.

Similar to voltage sources, current sources are classified as follows :

i) Time Invariant Sources :

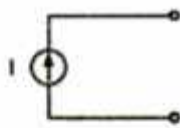


Fig. 1.19 (a) D.C. source

The sources in which current is not varying with time are known as **time invariant current sources** or **D.C. sources**. These are denoted by capital letters.

Such a current source is represented in the Fig. 1.19 (a).

ii) Time Variant Sources :

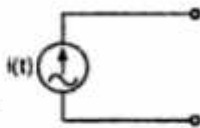


Fig. 1.19 (b) A.C. source

The sources in which current is varying with time are known as **time variant current sources** or **A.C. sources**. These are denoted by small letters.

Such a source is represented in the Fig. 1.19(b).

The sources which are discussed above are independent sources because these sources does not depend on other voltages or currents in the network for their value. These are represented by a circle with a polarity of voltage or direction of current indicated inside.

1.13.3 Dependent Sources

Dependent sources are those whose value of source depends on voltage or current in the circuit. Such sources are indicated by diamond as shown in the Fig. 1.20 and further, classified as,

i) Voltage Dependent Voltage Source : It produces a voltage as a function of voltages elsewhere in the given circuit. This is called **VDVS**. It is shown in the Fig. 1.20 (a).

ii) Current Dependent Current Source : It produces a current as a function of currents elsewhere in the given circuit. This is called **CDCS**. It is shown in the Fig. 1.20 (b).

iii) Current Dependent Voltage Source : It produces a voltage as a function of current elsewhere in the given circuit. This is called **CDVS**. It is shown in the Fig. 1.20 (c).

iv) Voltage Dependent Current Source : It produces a current as a function of voltage elsewhere in the given circuit. This is called **VDCS**. It is shown in the Fig. 1.20 (d).

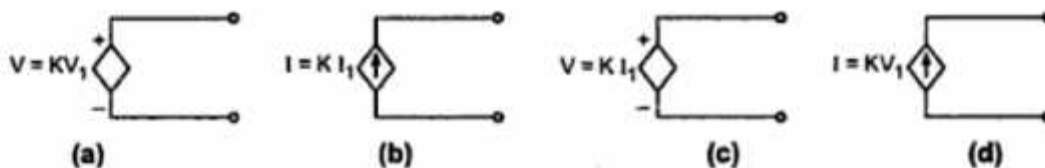


Fig. 1.20

K is constant and V_1 and I_1 are the voltage and current respectively, present elsewhere in the given circuit. The dependent sources are also known as controlled sources.